

(i) Printed Pages : 3

Roll No.

(ii) Questions : 9

Sub. Code :

2	6	1	0	8
---	---	---	---	---

Exam. Code :

0	4	7	3
---	---	---	---

M.Sc. Physics 2nd Semester
(2055)

ELECTRONICS-II

Paper : PHY-8024

Time Allowed : Three Hours]

[Maximum Marks : 60

Note :— Attempt **five** questions in all, selecting **one** question from each unit (Unit I to IV). Question No. **9** of the Unit-V is compulsory.

UNIT—I

1. (a) Minimize the following logic function in term of minterm and don't-care conditions. Also realize using NAND gates :
$$f(A, B, C, D) = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$$
 7
- (b) Explain the working of 3 I/P and 3 O/P PLA architecture with a diagram. Also construct seven segment outputs for four input variables. 5
2. (a) What do you understand by logic family ? Write down different performance characteristics of logic family. 7
- (b) Realise the following function of four variables using 4 to 16 line decoder with active-low outputs :
$$f(A, B, C, D) = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$$
 5

UNIT—II

3. (a) Differentiate between asynchronous and synchronous counter. Discuss synchronous decade counter with appropriate sequence. 6
- (b) Design ripple counter for 4 bit down counter using flip flop. Draw proper sequence and waveforms for it. 6
4. (a) Discuss master slave J-K flip flop to overcome race round condition of S-R flip flop. Explain the method with the help of diagram. 6
- (b) What is D type flip flop ? Convert D flip flop into T type flip flop. 6

UNIT—III

5. (a) Explain the working of successive approximation and counting type analog to digital converter. 9
- (b) Define accuracy and resolution of A/D converter. How many bits are required in binary ladder to achieve a resolution of 1 mV if full scale is + 5 V ? 3
6. Write the details on :
- (a) Classification of various memories of storage.
- (b) Charge coupled memory devices system along with their useful applications. 6,6

UNIT—IV

7. (a) Describe the epitaxial growth and masking and etching process in the IC fabrication. 8
- (b) Explain the details of any **four** of following :
- (i) SUI
 - (ii) RAL
 - (iii) LXI
 - (iv) CMP
 - (v) JMP
 - (vi) PUSH 4
8. (a) Give details of organization and operation of 8085A microprocessor. 6
- (b) Discuss various addressing modes of instruction 8085 with examples. 6

UNIT—V

9. Give the point answers of following questions :
- (a) Convert 1100 decimal to octal and hexadecimal system.
 - (b) What is switch contact bounce circuit ?
 - (c) What is linearity error in digital to analog converter ?
 - (d) What is parity generator ?
 - (e) How long will it take to shift 7 bit number into SIPO shift register if clock is set at 20 KHz ?
 - (f) What is the difference between data bus and address bus ? $6 \times 2 = 12$